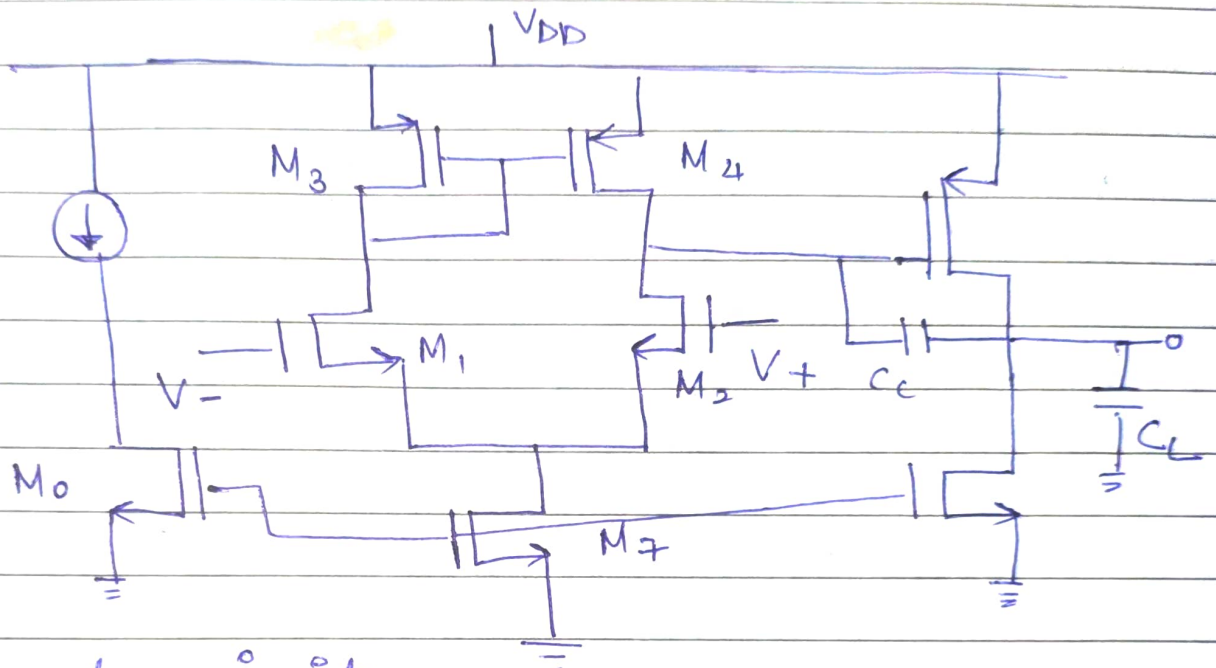



Project Report

Eklavya Jain
240102103

Circuit Diagram



Preferred circuit

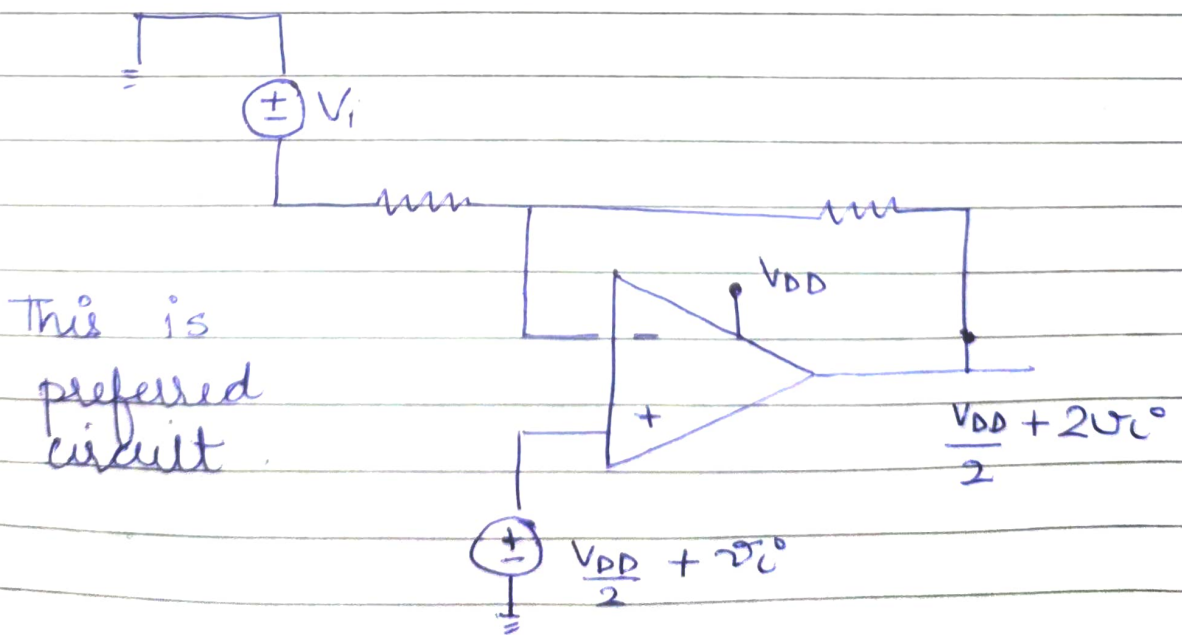

Specifications

- i) at least 40dB (taking 60dB) of DC gain
- ii) GBW = 5 MHz
- iii) PM $\geq 60^\circ$
- iv) Slew rate $\geq 10V/\mu\text{sec}$
- v) ICMR (+) = 1.6V ICMR (-) = 0.8V
- vi) Let's take $C_L = 10\text{pF}$
- vii) $V_{DD} = 1.8V$
- viii) $\mu_{n\text{cox}} = 200 \mu\text{A}/V^2$ (initially)
 $\mu_{p\text{cox}} = 100 \mu\text{A}/V^2$ (initial)

Calculations

→ Slew rate = $\frac{I_7}{C_C}$ and for $\geq 60^\circ$ phase margin.

$C_C = 0.4C_L = 4\text{pF}$ $I_7 \geq 40\mu\text{A}$

• M_1 & M_2

→ $g_{m1} = \text{GBW} \cdot C_C \cdot 2\pi = 40\pi \mu\text{S} = 125 \mu\text{S}$

→ $\left(\frac{W}{L}\right)_1 = \frac{g_{m1}^2}{\mu_{n\text{cox}} I_{D7}} = 1.69$

→ $\mu_{n\text{cox}} \left(\frac{W}{L}\right)_1 = 1.69$

→ $\sqrt{\frac{I_{D5}}{\beta_3}} = V_{DD} - |V_{th3}| + V_{th1} - V_{in\text{max}}$

$\left(\frac{W}{L}\right)_{3/4} = \frac{I_5}{\mu_{p\text{cox}} (V_{DD} - |V_{th3}| + V_{th1} - V_{in\text{max}})^2}$

$$\left(\frac{W}{L}\right)_{3,4} = 20.40$$

Since $I_7 \geq 40 \mu A$ and $I_{ref} = 4$ so 10 times current. So, factor is ≥ 10 .
Assume $\left(\frac{W}{L}\right)_{M_0} = 2$. then we must

$$\text{have } \left(\frac{W}{L}\right)_7 \geq 2 \times 10 = 20.$$

I took it be 40 for good gain for reasonable phase margin ($\sim 60^\circ$).

$$g_{m5} = 2.2 g_{m4} \left(\frac{C_L}{C_c}\right)$$

$\Delta \quad g_{m5} \gg 10 g_{m1}$

$$V_{SG4} = V_{SG} = 5$$

$$\hookrightarrow \left(\frac{W}{L}\right)_5 = \left(\frac{W}{L}\right)_4 \left(\frac{g_{m5}}{g_{m4}}\right)$$

$$\left(p_2 = \frac{g_{m5}}{2\pi C_L}\right) \text{ (Comes from 2nd stage).}$$

$$\therefore p_2 \geq 11 \text{ MHz}$$

$$11 \times 10^6 = \frac{g_{m5}}{2\pi C_L}$$

$$g_{m5} \geq 697 \mu S$$

Now since overdrive in both are same -
 $V_{SG} - |V_{th}|$ are same both M_4 and M_5 .

$$g_{m4} = \sqrt{2\mu_p C_{ox} \left(\frac{W}{L}\right)_4 I_{D4}} = 286 \mu S$$

$$\Delta V_{D4} = \frac{2I_{D4}}{g_{m4}} = 0.14 V$$

So for better phase margin we already got

$$g_{m5} \approx 6911 \text{ mS}$$

we must have $\Delta V_5 = \Delta V_6 = 0.14 \text{ V}$

$$g_{m5} = \frac{2I_{D5}}{V_{ov5}}$$

$$I_{D5} = 48.37 \text{ (}\mu\text{A)}$$

Let's assume ($\approx 55 \text{ m}\mu\text{A}$)

$$\left(\frac{W}{L}\right)_5 = 56.2375$$

$$W = 25.551 \text{ }\mu\text{m} \quad L = 0.451 \text{ }\mu\text{m}$$

now M_6 must be able to pull this current off

$$\left(\frac{55}{4}\right) = \text{multiplier}$$

$$\frac{55}{4} \times 1.69 \approx \frac{55}{4} \times 2 = 27.5 = \left(\frac{W}{L}\right)_6$$

Let's check what we get from LT spice :-

i) dc gain :- 64.783 dB ($\geq 60 \text{ dB}$)

ii) P.M at $0 \text{ dB} = 65^\circ$

iii) GBW = 4.7 MHz

iv) Currents in each transistor

All are dc currents.

$$M_0 = 4 \mu\text{A}$$

$$M_2 = 27.74 \mu\text{A}$$

$$M_4 = 27.74 \mu\text{A}$$

$$M_1 = 27.87 \mu\text{A}$$

$$M_3 = 27.87 \mu\text{A}$$

$$M_7 = 55.62 \mu\text{A}$$

$$M_5 = 46.8984 \mu\text{A}$$

$$M_6 = 46.8984 \mu\text{A}$$

now $r_o = \frac{1}{\lambda I_D}$ & $g_m = \sqrt{2\mu_n C_{ox} \frac{W}{L} I_D}$

Date : _____
Page : _____

80

T_x No	$r_o (K\Omega)$	$g_m (\mu s)$	ΔV	W/L	$I_D (\mu A)$	W	$L (\mu m)$
0	2500	60.7	0.132	2.6	4	1 μm	0.5
1	360	147	0.378	1.69	27.8	0.85 μm	0.5
2	360	147	0.378	1.69	27.8	0.85 μm	0.5
3	360	337.2	0.165	20.45	27.8	10.22 μm	0.5
4	360	337.2	0.165	20.45	27.8 46.9	10.22 μm	0.5
5	180	1011.6	0.110	40	46.9	26.55 μm	0.5
6	213	692.3	0.135	51.1	46.9	12.5 μm	0.5
7	213	734.4	0.128	25.5	55.5	20 μm	0.5

GBW

PM $\approx 65^\circ$

Cursor 1

V(n004)


Freq:	4.7962176MHz	Mag:	-252.70729mdB	☒
		Phase:	-116.34628°	☐
		Group Delay:	12.406939ns	☐

Cursor 2

Freq:	-- N/A --	Mag:	-- N/A --	☐
		Phase:	-- N/A --	☐
		Group Delay:	-- N/A --	☐

Ratio (Cursor2 / Cursor1)

Freq:	-- N/A --	Mag:	-- N/A --
		Phase:	-- N/A --
		Group Delay:	-- N/A --

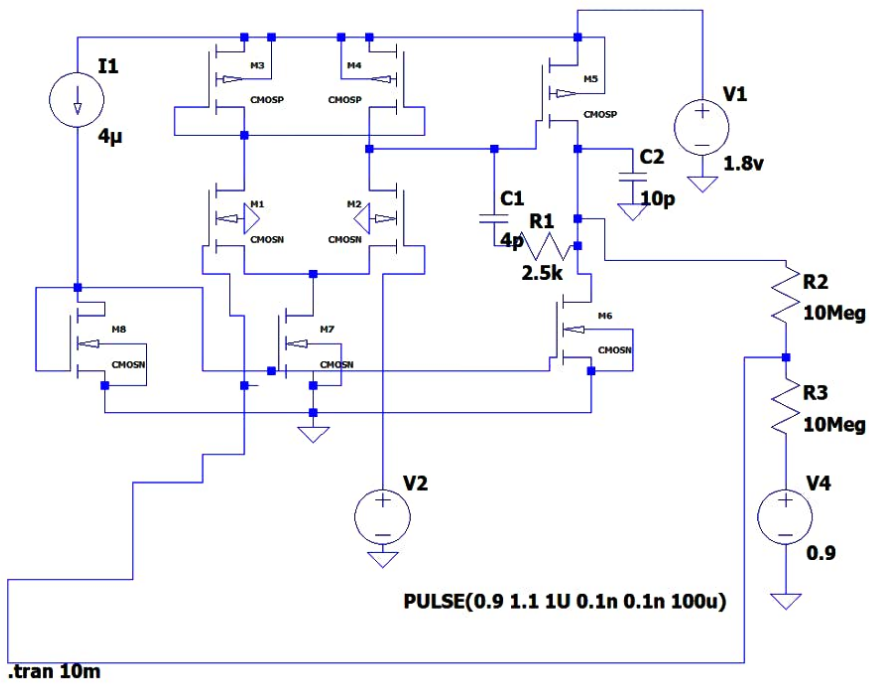

.include tsmc018.lib

.ac dec 100 0.1 100Meg

Operating Points

V(n001) :	1.8	voltage
V(n002) :	1.15744	voltage
V(n003) :	1.19874	voltage
V(n004) :	0.902604	voltage
V(n005) :	0.9	voltage
V(n006) :	0.902604	voltage
V(n007) :	0.901302	voltage
V(n008) :	0.0849597	voltage
V(n009) :	0.557781	voltage
V(n010) :	0.9	voltage
I(C1) :	1.18453e-24	device_current
I(C2) :	9.02604e-24	device_current
I(I1) :	4e-06	device_current
I(R1) :	0	device_current
I(R2) :	1.30188e-10	device_current
I(R3) :	1.30188e-10	device_current
I(V1) :	-0.000106646	device_current
I(V2) :	0	device_current
I(V4) :	1.30188e-10	device_current
Ib(M1) :	-1.26203e-12	device_current
Ib(M2) :	-1.30332e-12	device_current
Ib(M3) :	6.52559e-13	device_current
Ib(M4) :	6.11263e-13	device_current
Ib(M5) :	9.07396e-13	device_current
Ib(M6) :	-9.12604e-13	device_current
Ib(M7) :	-9.45853e-14	device_current
Ib(M8) :	-5.67781e-13	device_current

Ib (M8) :	-5.67781e-13	device_current
Id (M1) :	2.79511e-05	device_current
Id (M2) :	2.78263e-05	device_current
Id (M3) :	2.79511e-05	device_current
Id (M4) :	2.78263e-05	device_current
Id (M5) :	4.68687e-05	device_current
Id (M6) :	4.68686e-05	device_current
Id (M7) :	5.57773e-05	device_current
Id (M8) :	4e-06	device_current
Ig (M1) :	0	device_current
Ig (M2) :	0	device_current
Ig (M3) :	-0	device_current
Ig (M4) :	-0	device_current
Ig (M5) :	-0	device_current
Ig (M6) :	0	device_current
Ig (M7) :	0	device_current
Ig (M8) :	0	device_current
Is (M1) :	-2.79511e-05	device_current
Is (M2) :	-2.78263e-05	device_current
Is (M3) :	-2.79511e-05	device_current
Is (M4) :	-2.78263e-05	device_current
Is (M5) :	-4.68687e-05	device_current
Is (M6) :	-4.68686e-05	device_current
Is (M7) :	-5.57773e-05	device_current
Is (M8) :	-4e-06	device_current

